



80 Pages
27.6 cm x 21.2 cm

Ruled 7 mm • Ligné 7 mm

EXERCISE BOOK CAHIER D'EXERCICES

 NAME/NOM _____

SUBJECT/SUJET ELEC 201



ASSEMBLED IN CANADA WITH IMPORTED MATERIALS
ASSEMBLÉ AU CANADA AVEC DES MATIÈRES IMPORTÉES

12107



Overview

9/5/18

Reference Book

- "Fundamentals of Electric Circuits" - McGraw-Hill 6th ed.
Alexander and Sadiku
- DeCarlo and Lin "Linear Circuit analysis" Oxford 2nd ed.

office hours Virtual google meet

<http://tinyurl.com/11-Office-hours>
Kaiser 3025

google docs poll
give
CWL ID not password
and email

LEC 1

9/7/18


ECT is a language

- Charge
- Current
- Voltage

Current (Flow of charge at a point)

$$\begin{array}{c} \xleftarrow{3C/s} \ominus \\ \oplus \xrightarrow{7C/s} \\ = \oplus \xrightarrow{10C/s} \\ \text{or} \\ 10A \end{array}$$

$$i = \frac{dq}{dt}$$

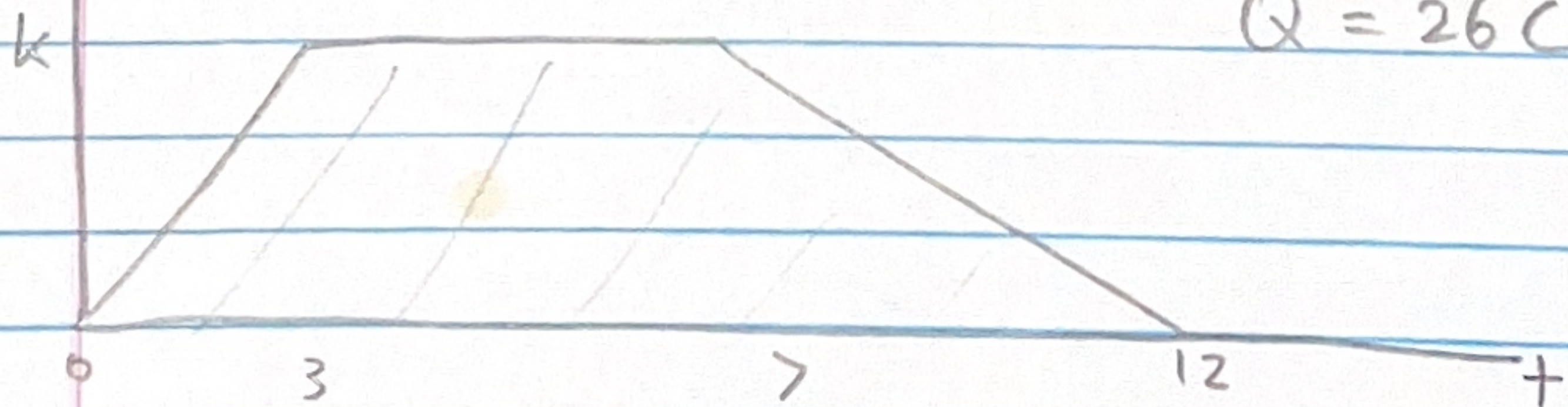


$$\frac{3k}{2} + 4k + \frac{5k}{2} = 26$$

$$k \left(\frac{3}{2} + 4 + \frac{5}{2} \right) = 26$$

$$\therefore k = 3.25$$

$$i(t) = 5 \cos(300t) \text{ A}$$

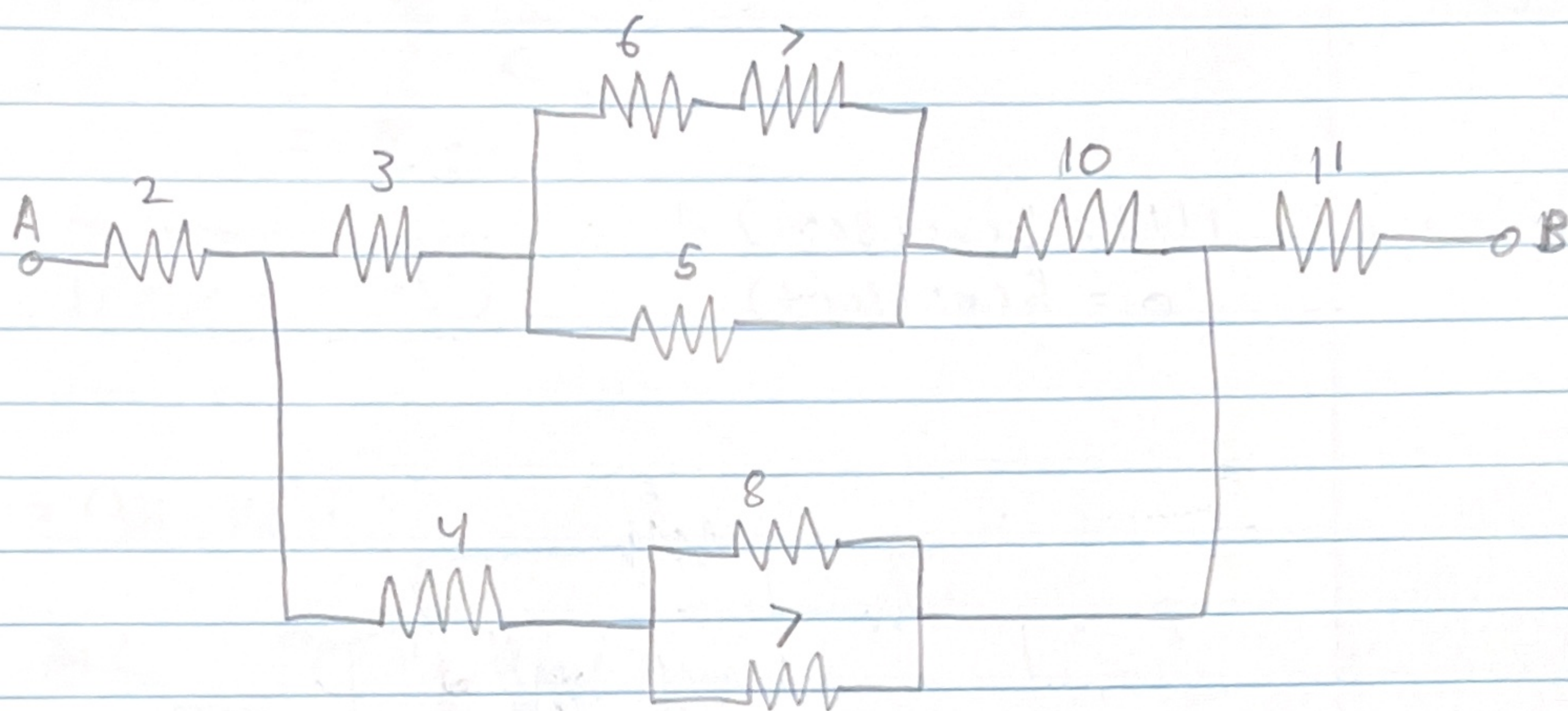

$$R_{eq} = 2 + R(4 + R(8, 9), 3 + R((6 + 7, 5) + 10) + 11)$$


9/12/18

LEC

Example

$$i(t) = 5 \cos(300t) \text{ A}$$


$$v(t) = 5 \cos(300t)$$

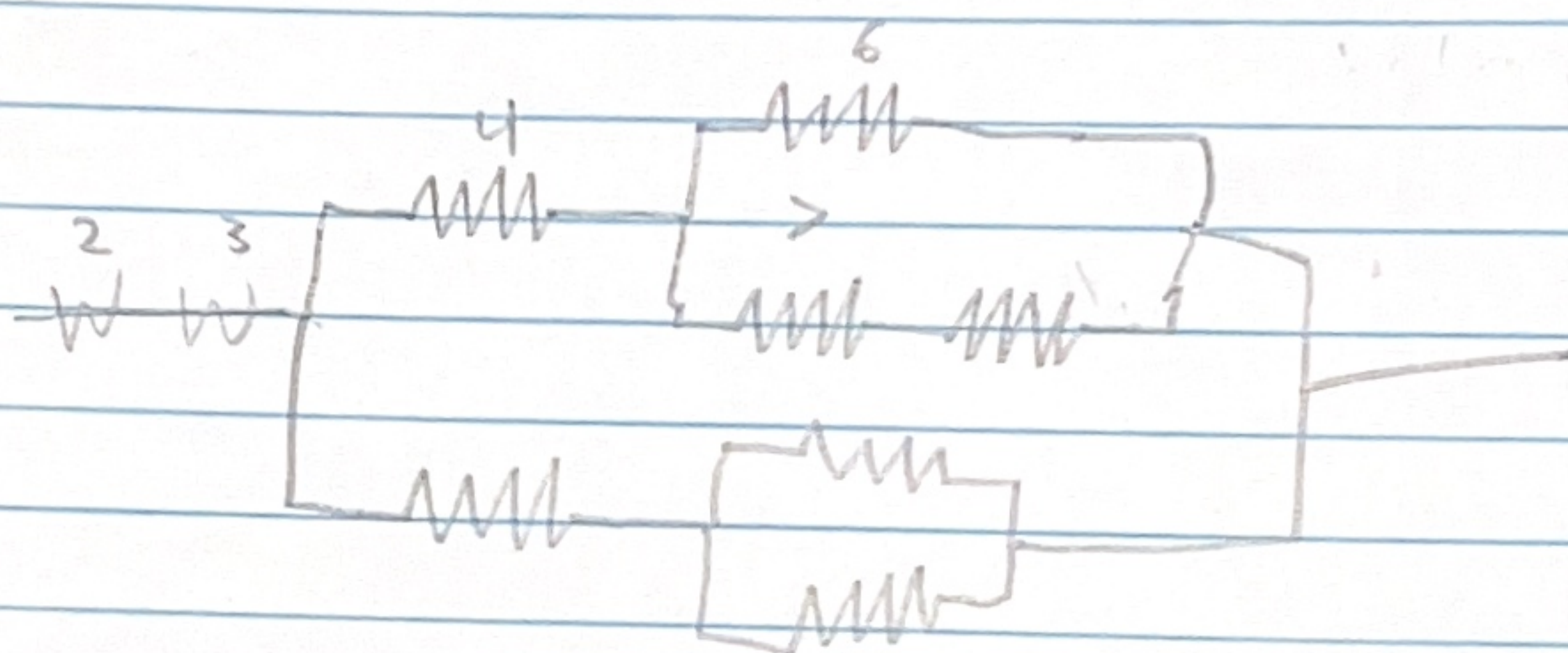

8.2

Voltage

- Difference of electric potential

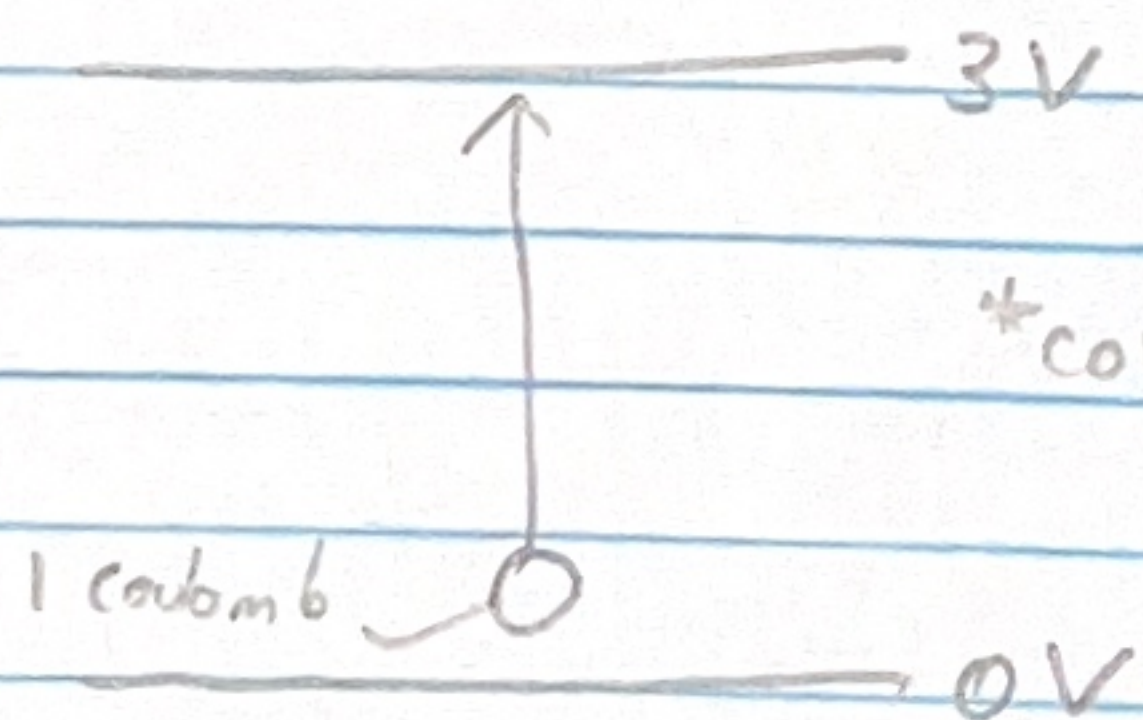

*costs 3J to do this

$$V = J/C$$

$$\text{Power} = \frac{C}{s} \cdot \frac{J}{C}$$

$$= J/s$$

$$\boxed{\text{Power} = iV}$$

$$P = (V_o - V_d)i$$

$$\text{CALC: } PP(V_o, V_d, i)$$

Energy

$$W = \int p dt$$

Directions/Polarities / - sign

$$\xrightarrow{\oplus} = \xleftarrow{\ominus}$$

Components $\Rightarrow$ linear one pair of terminals

Elements

Active $\Rightarrow$ can deliver power ie: Batteries. called sources

Passive $\Rightarrow$ Absorb power ie: resistors

Reactive $\Rightarrow$ Store power and deliver back to the circuit ie: inductors, capacitors

Resistance $\Rightarrow$ opposition to currents i

Inductance $\Rightarrow$ opposition to changes in currents $\frac{di}{dt}$



Capacitance $\Rightarrow$ opposition to changes in voltages $\frac{dV}{dt}$

Ohm's Law

$$V = IR$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

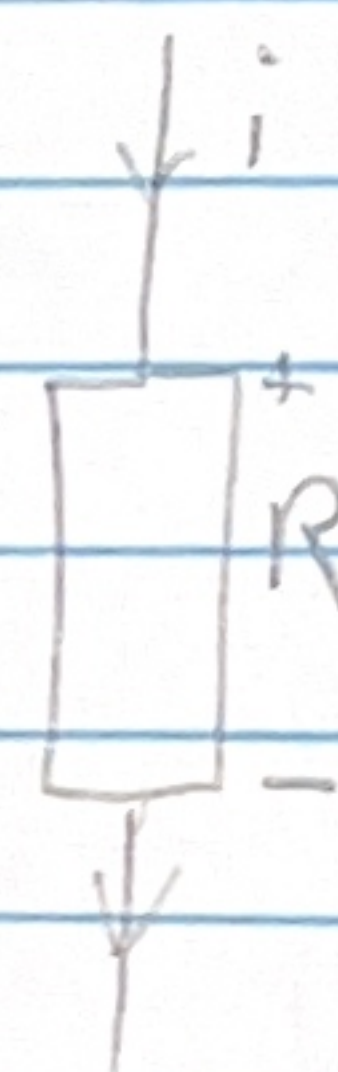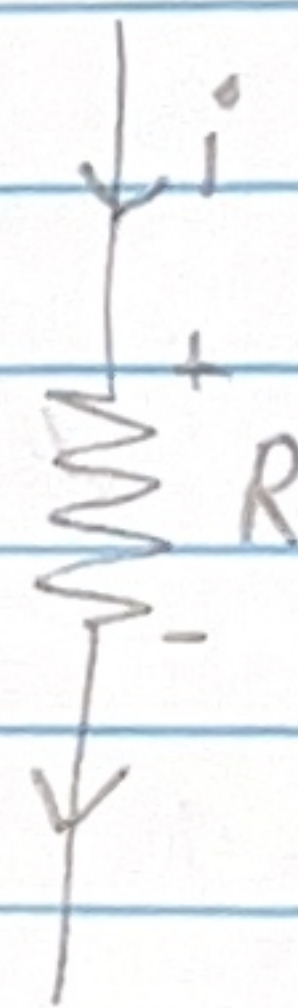

European

Conductance

$$G = 1/R \quad (\text{in Siemens } S)$$

$$i = GV$$

Inductance

$$V = L \frac{di}{dt} ; \quad \frac{di}{dt} = \frac{V}{L} ; \quad i = \frac{1}{L} \int v dt$$

L in Henrys (H)

Capacitance

C in Farads (F)

$$i = C \frac{dv}{dt}$$

$$V = \frac{q}{C}$$

$$V = \frac{1}{C} \int i dt$$

$$q = CV$$

Resistors 2 Parameters

① Resistance

② Power Threshold

Inductors 2 Parameters

① Inductance

② Current threshold

Capacitors 2 Parameters

① Capacitance

② Voltage threshold

Active Sources

① Independent





-Values don't depend on current/voltage

② Dependent/Controlled



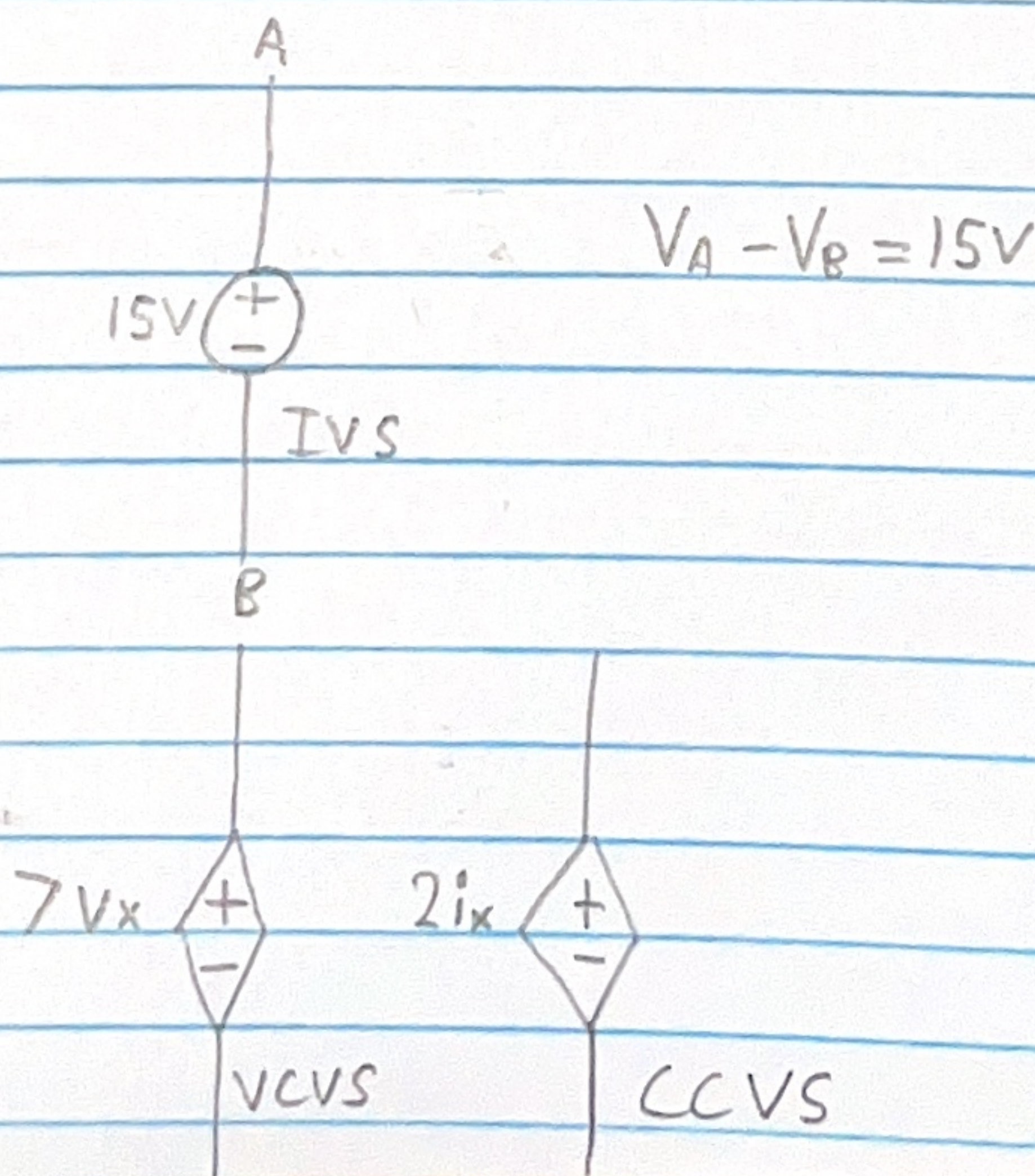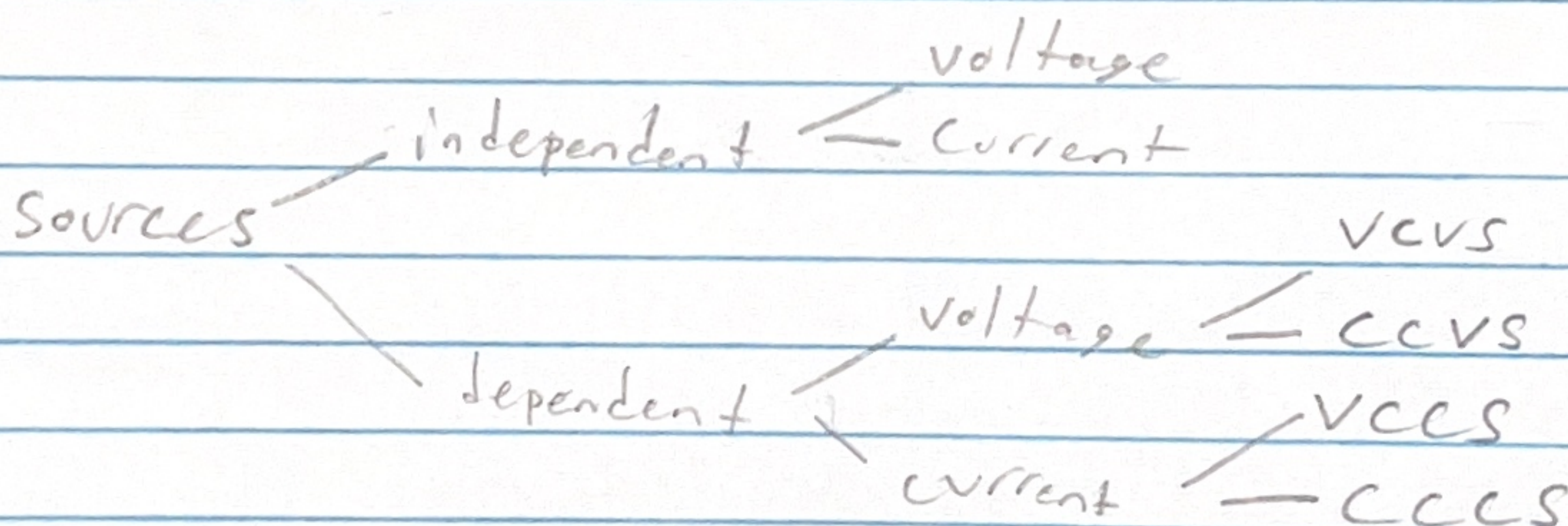-Values depend on current/voltage in the circuit



9/19/18

LEC




q C

i C/s







V J/C


P $W = iV$

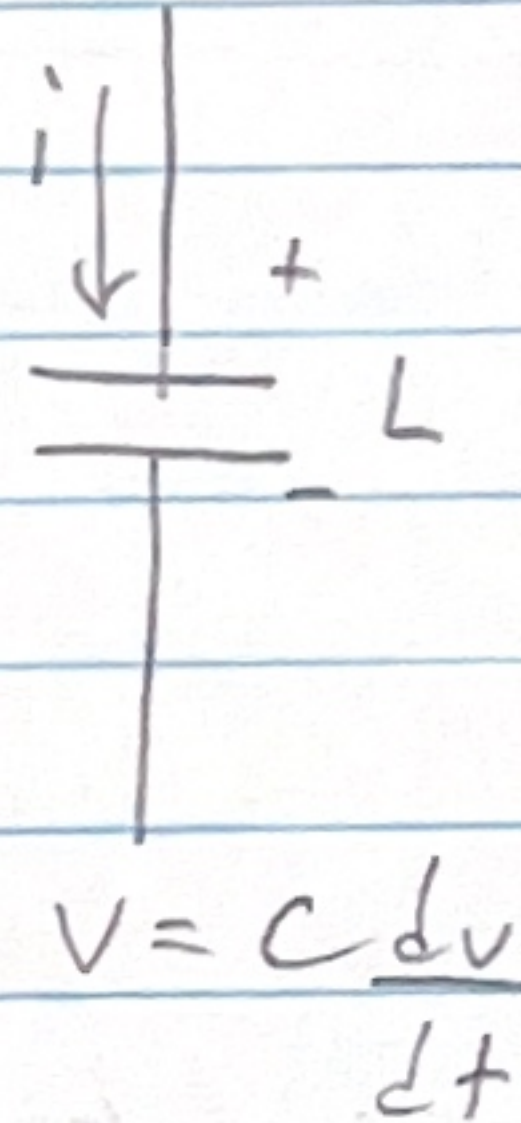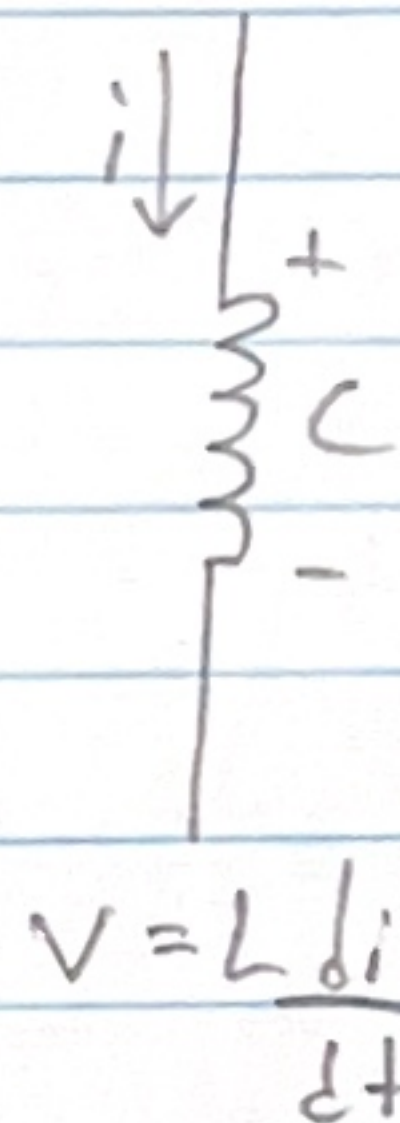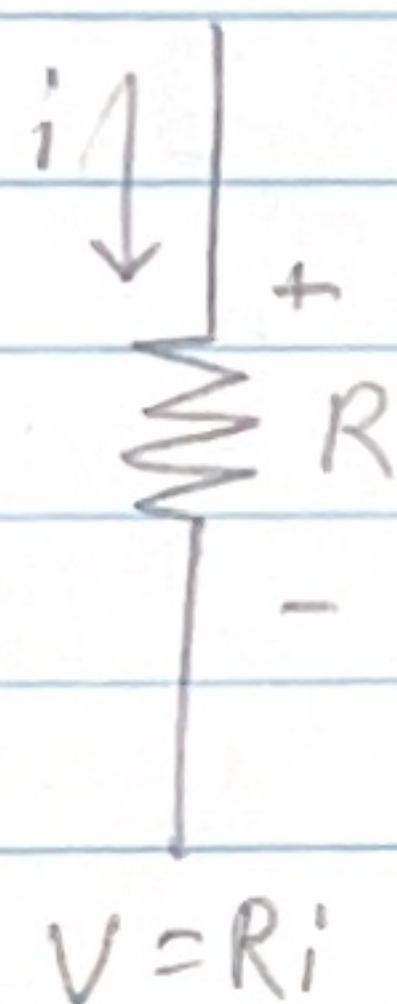- Current flowing downhill is absorbing i.e. resistor
- uphill is delivering power



Sources (Ideal) //round

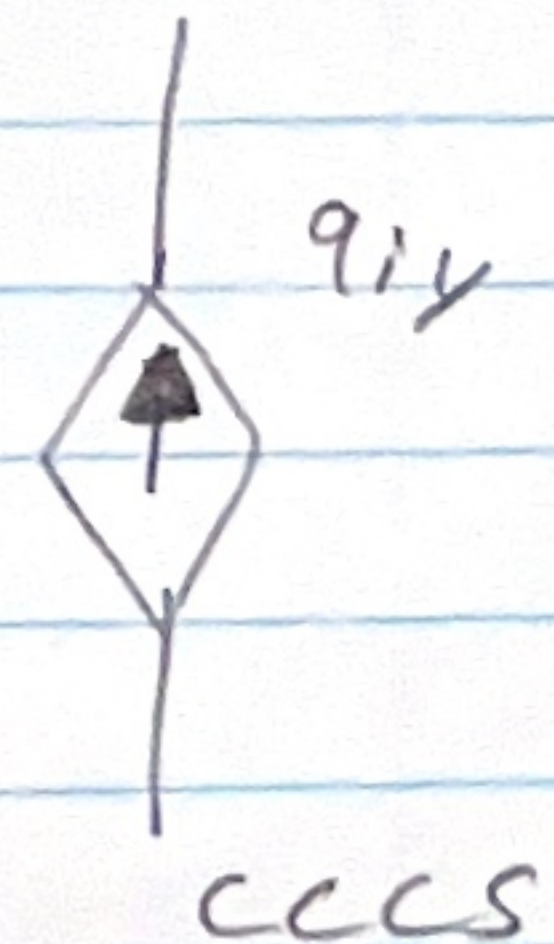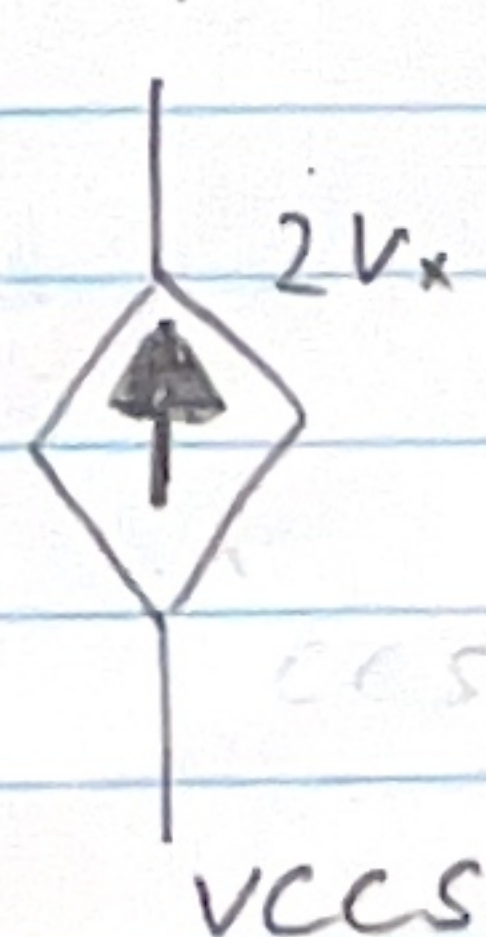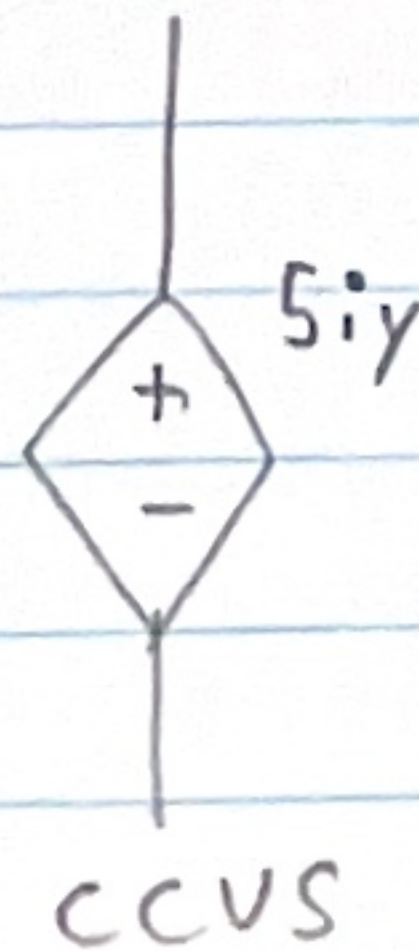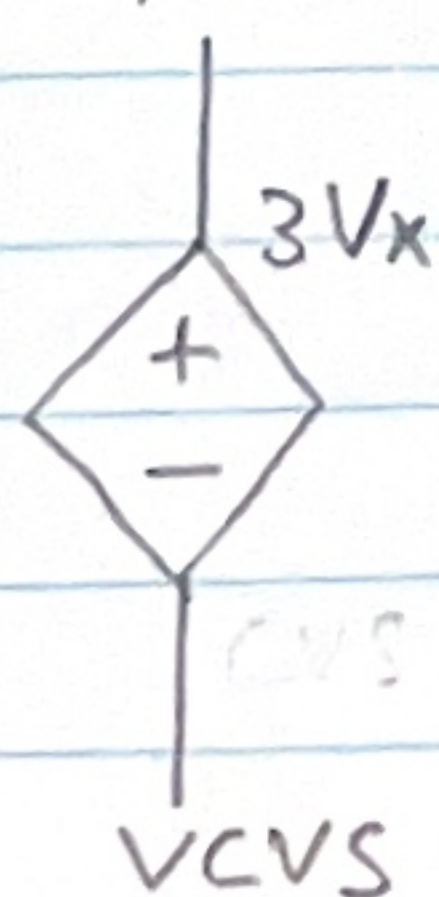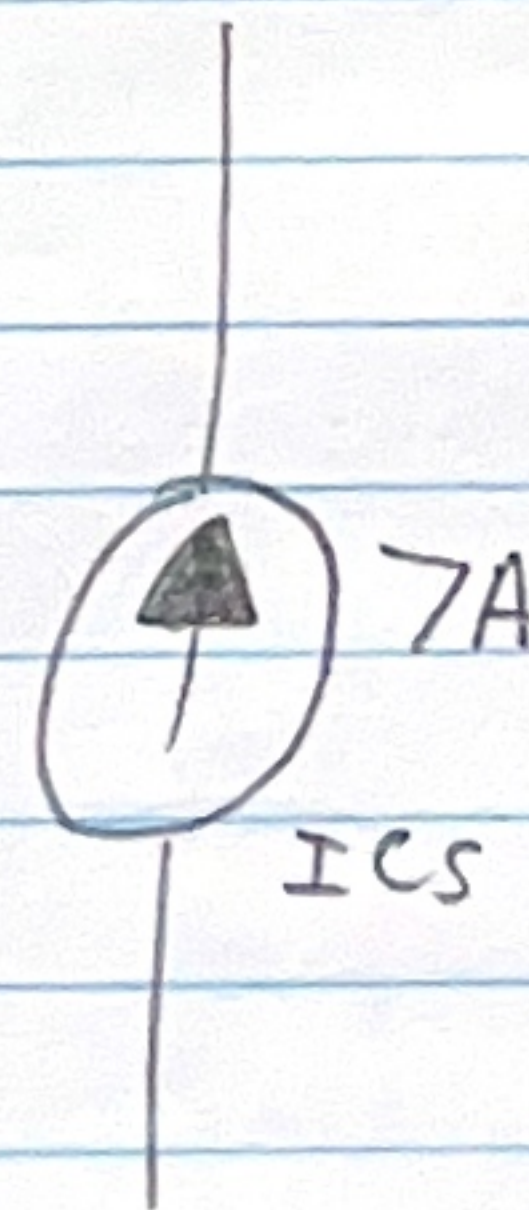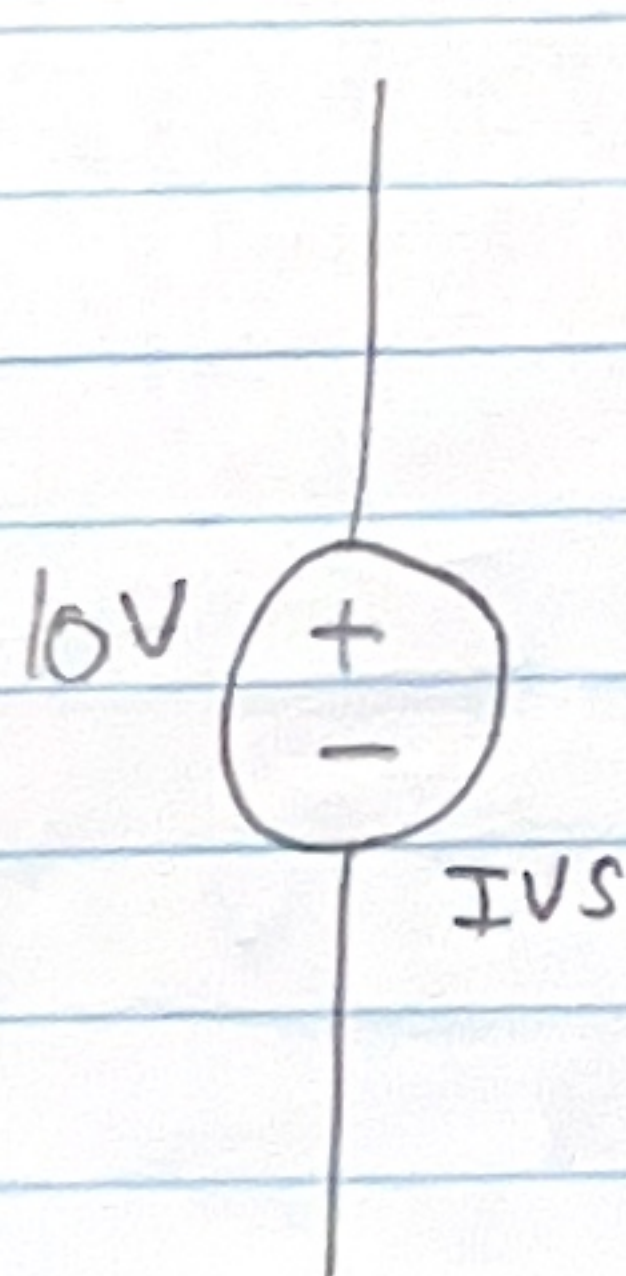

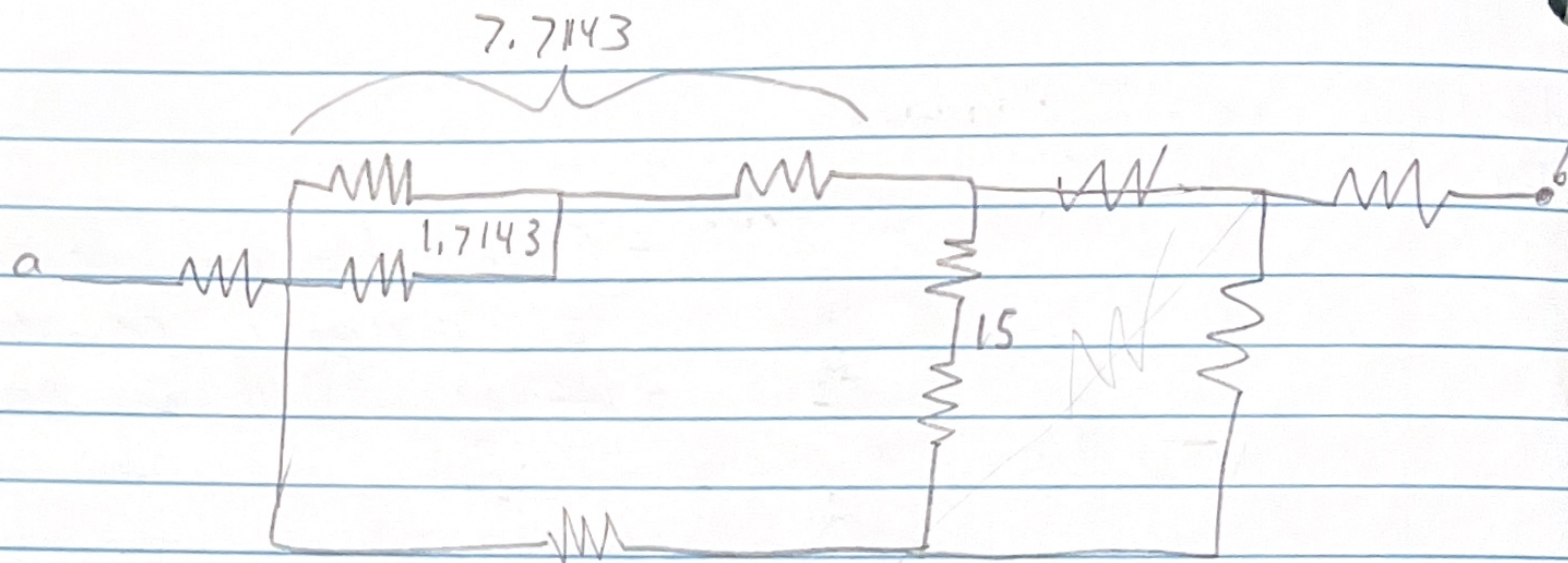


Kirchoff's Laws

KVL (Voltage Law)

$$\sum_{\text{loop}} V = 0$$

KCL (Current Law)

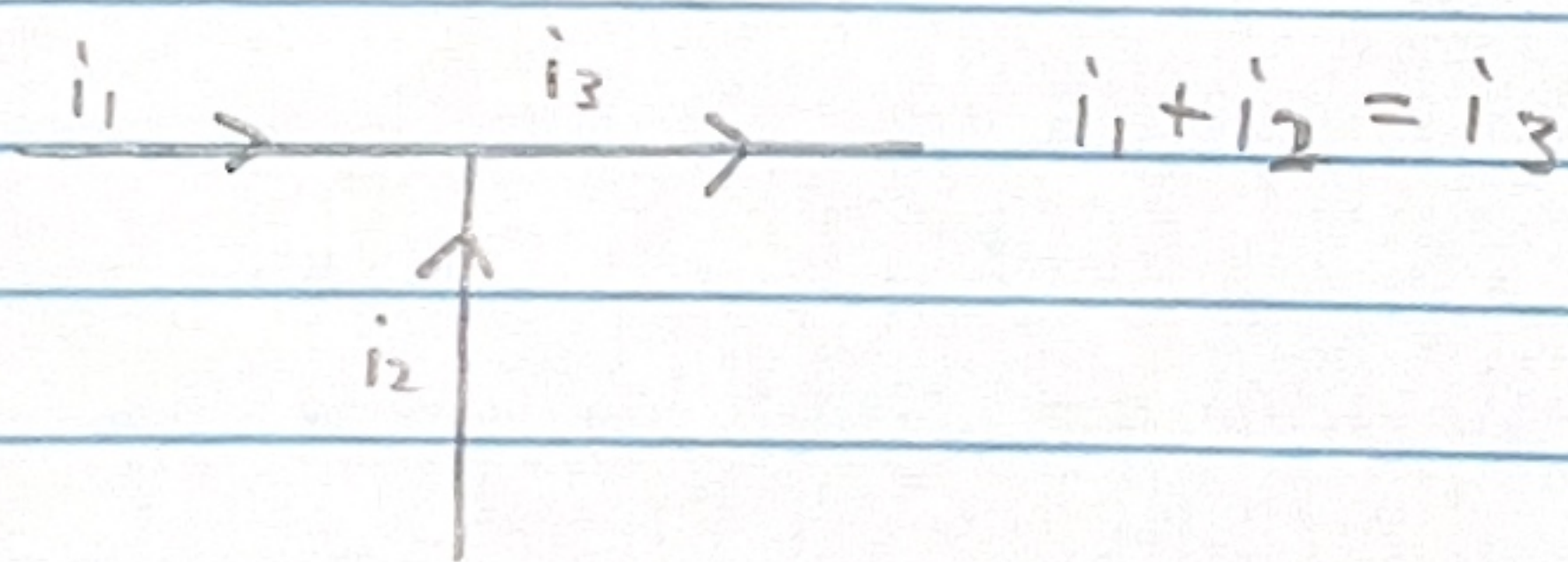

Types of Branches

R Branch



RV Branch




i branch



Ri Branch



Evil

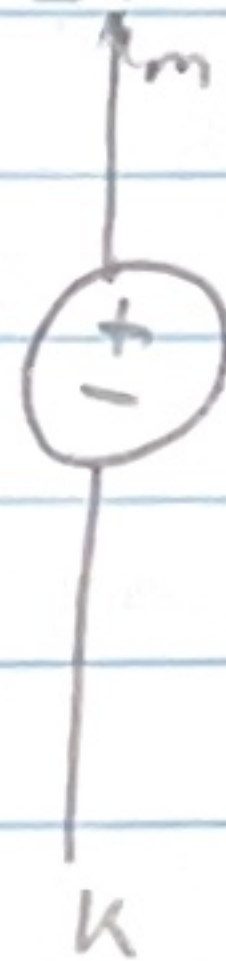

9/21/18
LEC

Current in R Branch

$$I = \frac{V_o - V_d}{R}$$

Current in RV Branch

$$I = \frac{V_o - V_d \pm V_s}{R} \quad \left\{ \begin{array}{l} +V_s : \text{Helping} \\ -V_s : \text{Opposing} \end{array} \right.$$


$\sqrt{1}$
must be
lower case



$$a = \frac{(\frac{1}{2})(\frac{1}{3})}{\frac{1}{2} + \frac{1}{3} + \frac{1}{4}} = 0.1538$$

$$c = \frac{(\frac{1}{3})(\frac{1}{4})}{\frac{1}{2} + \frac{1}{3} + \frac{1}{4}} = 0.1154$$
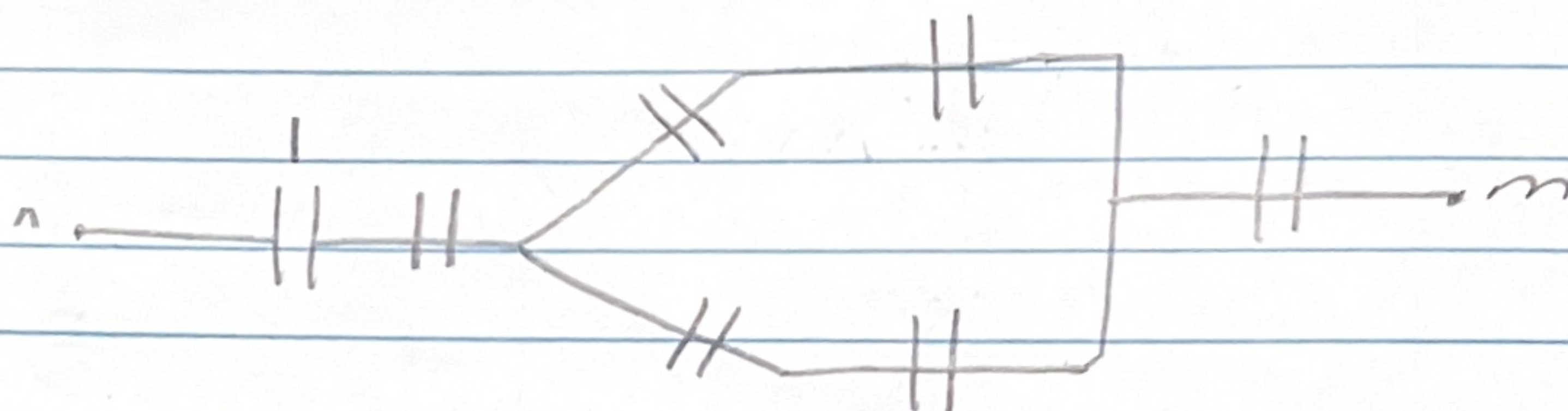
$$b = \frac{(\frac{1}{3})(\frac{1}{4})}{\frac{1}{2} + \frac{1}{3} + \frac{1}{4}} = 7.6923 \times 10^{-2}$$



Top Hat

$$V_1 = -1.11$$

$$i_x = 6.698412$$


$$V_2 = 29.381$$

$$V_y = 3.88$$

$$V_3 = 3.88$$

$$i_e = -0.3015873$$

9/26/18
LEC

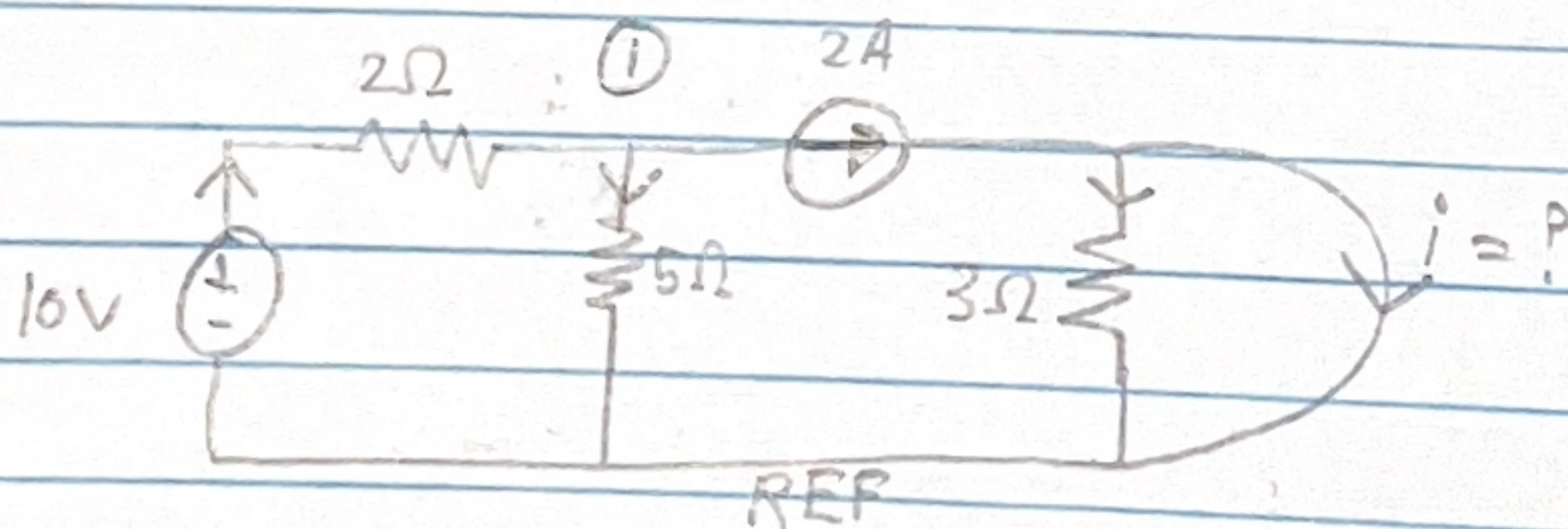

$$V_1: \frac{V_{REF} - V_1 + 10}{2} = \frac{V_1 - V_{REF}}{5} + 2$$

$$\frac{-V_1 + 10}{2} = \frac{V_1}{5} + 2$$

$$\frac{-V_1}{2} + 5 = \frac{V_1}{5} + 2$$


$$\frac{V_1}{5} + \frac{V_1}{2} = 3$$

$$\frac{2V_1}{10} + \frac{5V_1}{10} = 3$$

$$\frac{7V_1}{10} = 3$$

$$V_1 = \frac{10}{7}(3)$$


$$V_1 = \frac{30}{7} V$$

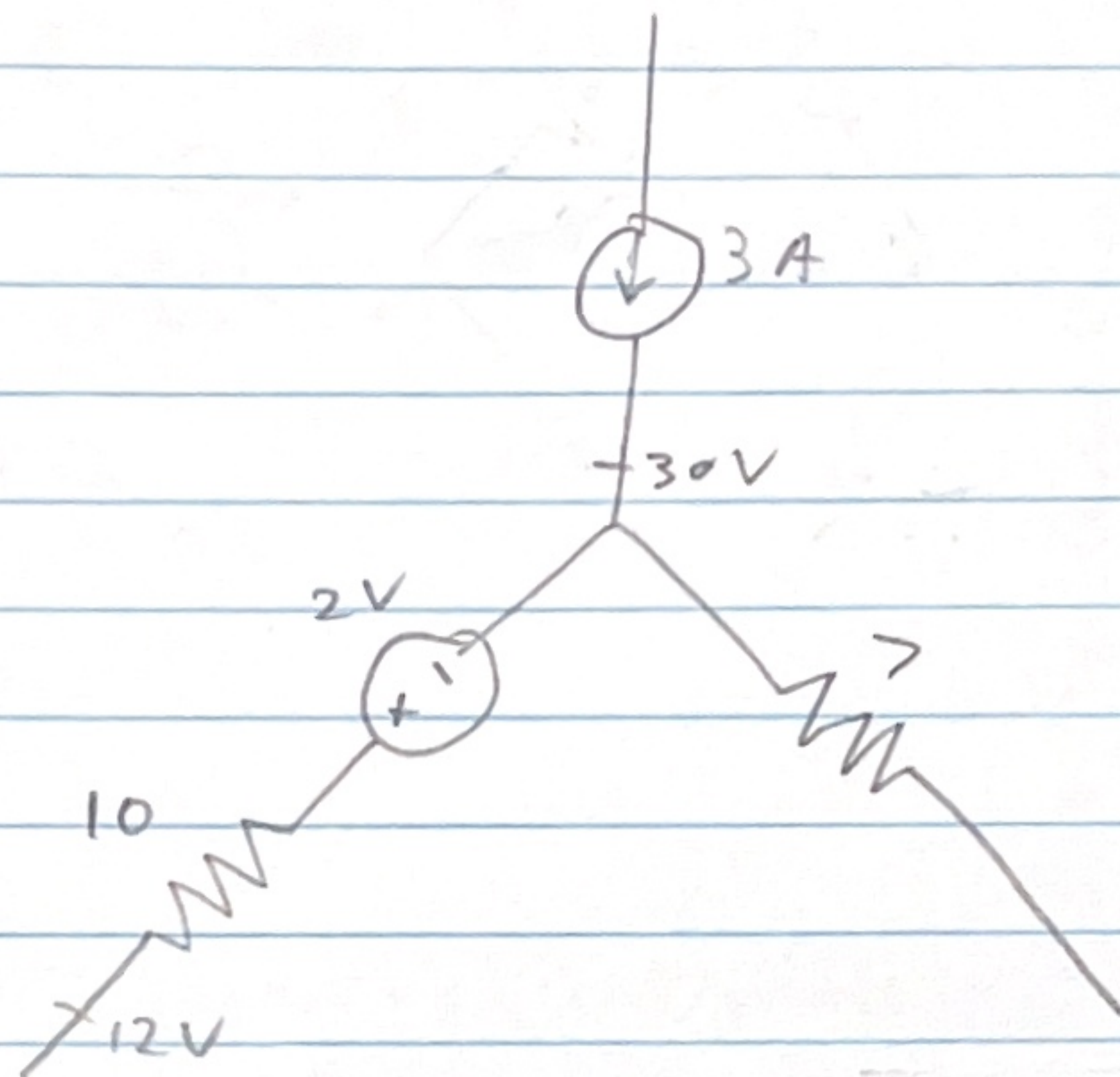

$$i = \frac{V}{R} = \frac{32 - 12}{10} =$$


$$\frac{(V_m + 2) - 10}{10} = i_1$$

$$i_2 = \frac{V_m - 20}{7}$$

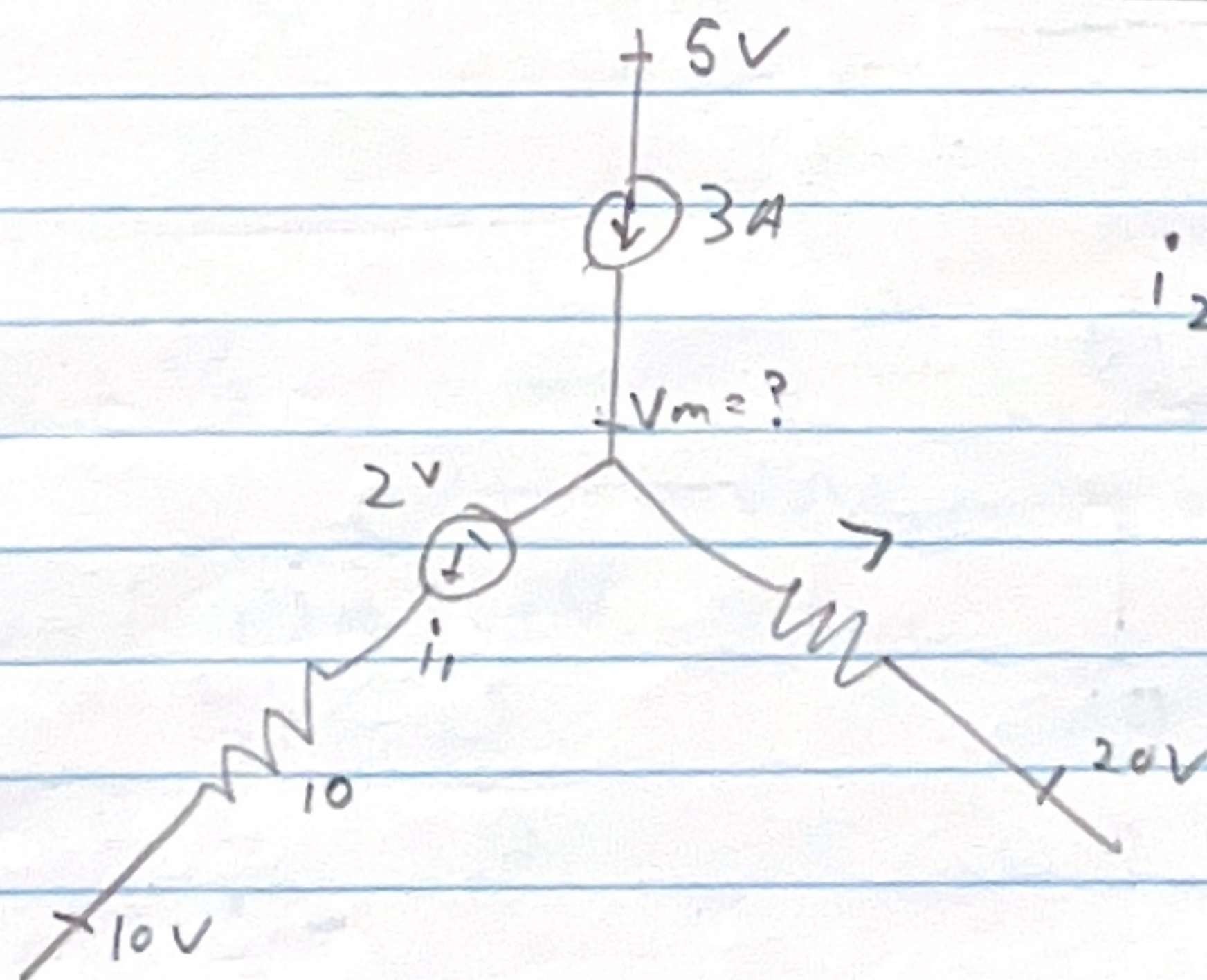

$$\frac{V_m - 20}{7} + \frac{V_m - 8}{10} = 3$$

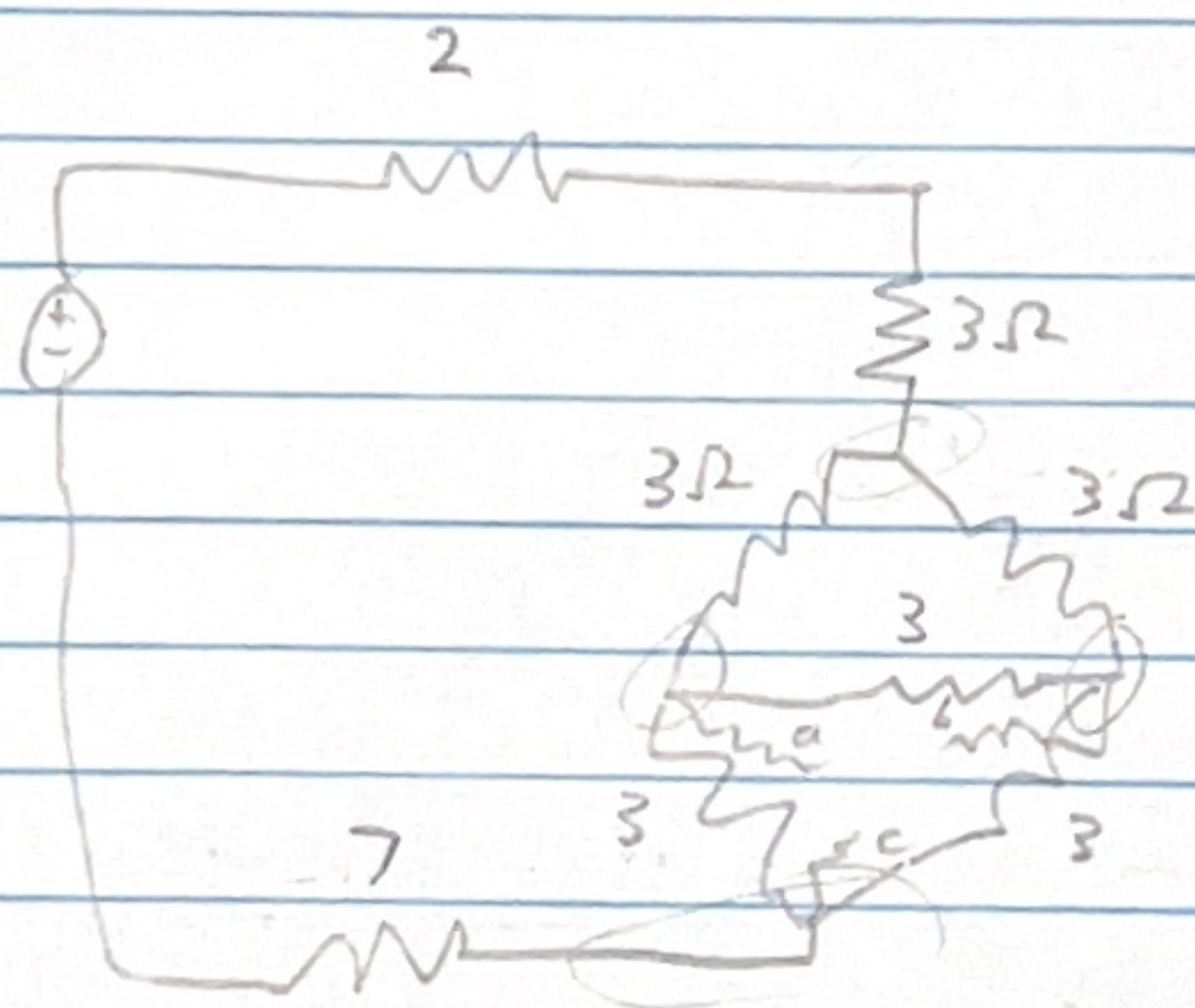
$$\frac{V_m}{7} - \frac{20}{7} + \frac{V_m}{10} - \frac{8}{10} = 3$$




$$b = c = a = \frac{(9)(9)}{27}$$

$$a, b, c = \frac{(3)(3)}{9}$$

$$= 1$$

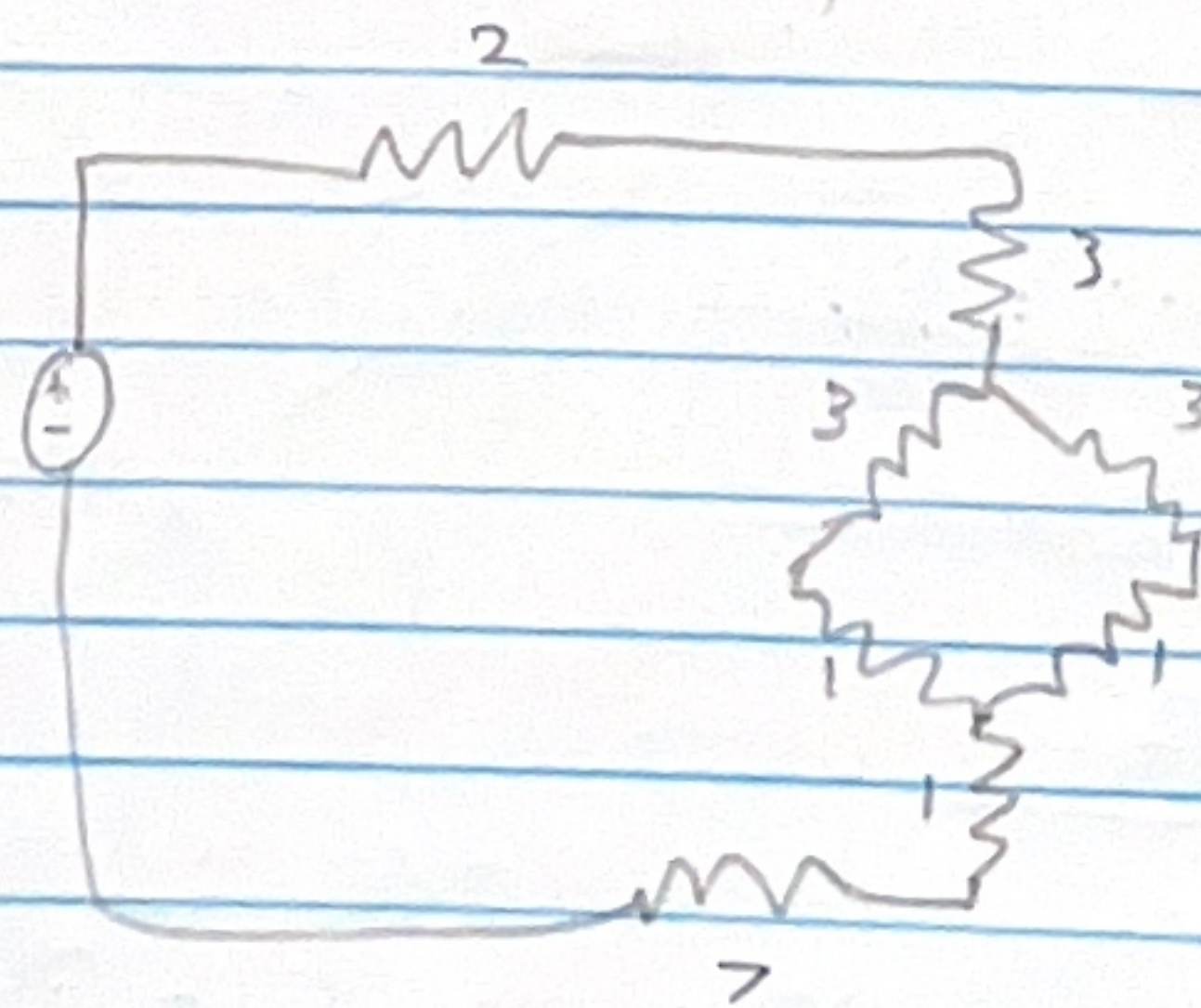

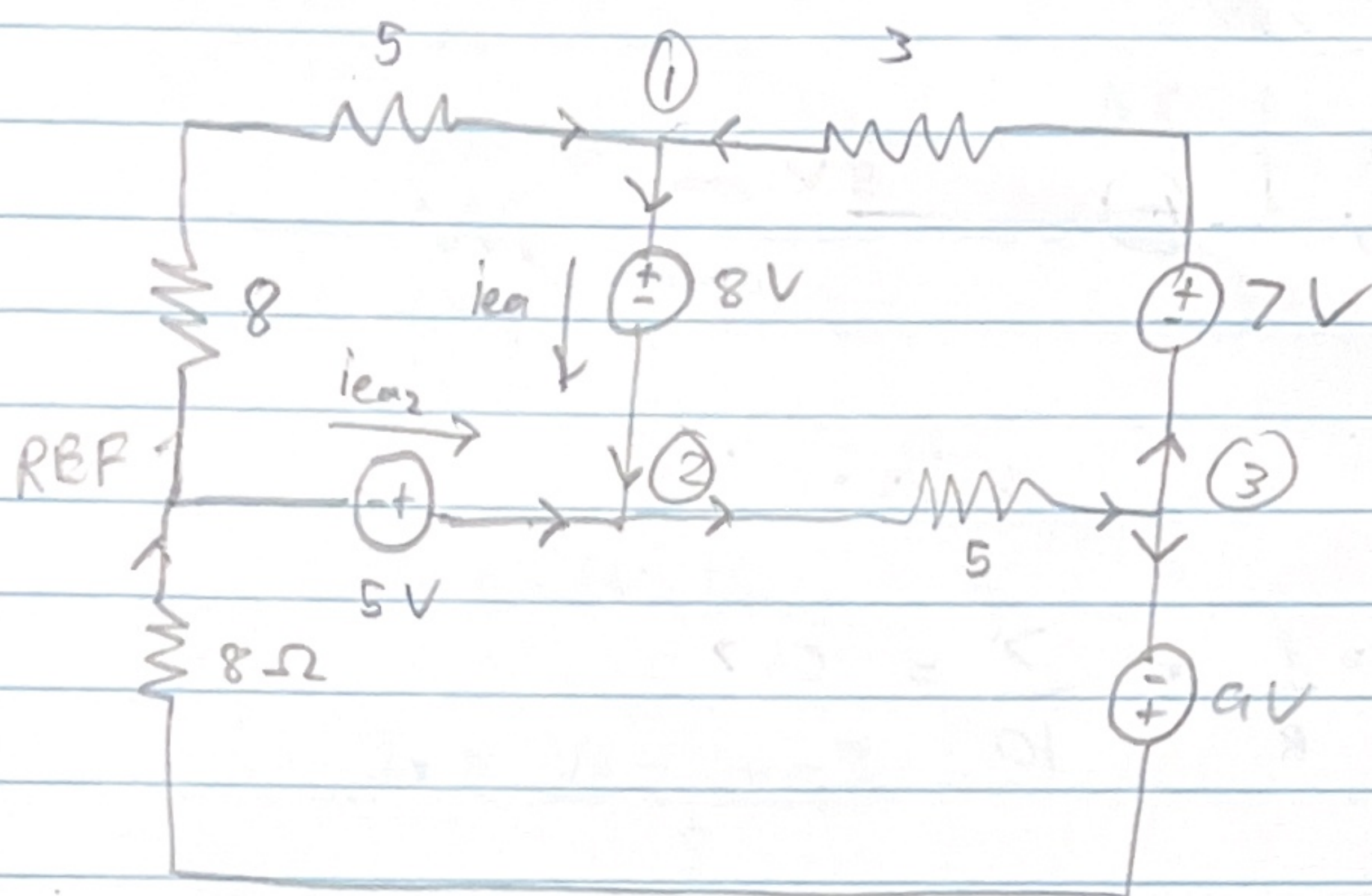

$$V_1: \frac{V_{REF} - V_1}{13} + \frac{V_3 - V_1 + 7}{3} = i_{ea}$$

$$V_2: i_{ea2} + i_{ea} = \frac{V_2 - V_3}{5}$$

$$V_3: \frac{V_2 - V_3}{5} = \frac{V_3 - V_1 + 7}{3} + \frac{V_3 - 0 + 9}{8}$$

$$i_{ea}: V_2 + 8 = V_1$$

Known

$$V_2 = 5V$$


$$i_{ea2}: 0 + 5 = V_2$$

$$A = V_1$$

$$B = V_3$$

$$C = i_{ea}$$

$$D = i_{ea2}$$

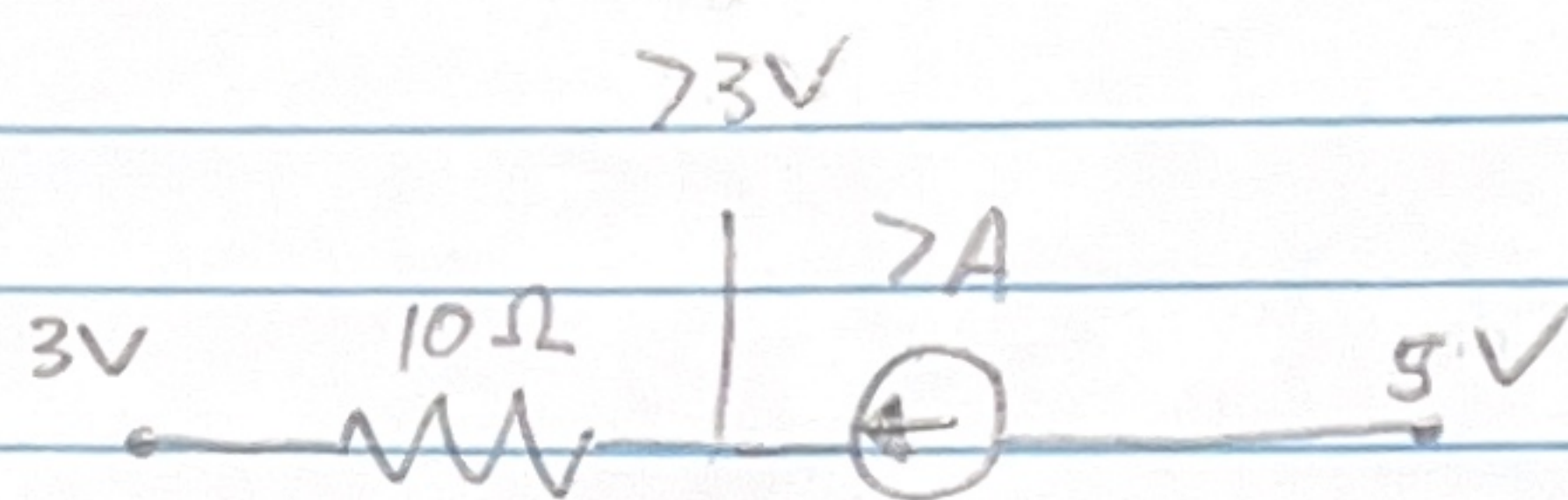

$$P_s = ?$$

$$V = \frac{i}{R} = \frac{7}{10} = 0.7$$


$$V = 5 - 3.7 = 1.3$$

$$\begin{aligned} P &= iV \\ &= (7)(1.3) \\ &= 9.1W \end{aligned}$$

$$V = IR = 70V$$

$$V = 5 - 73 = -68$$

$$P = iV = -68.7$$

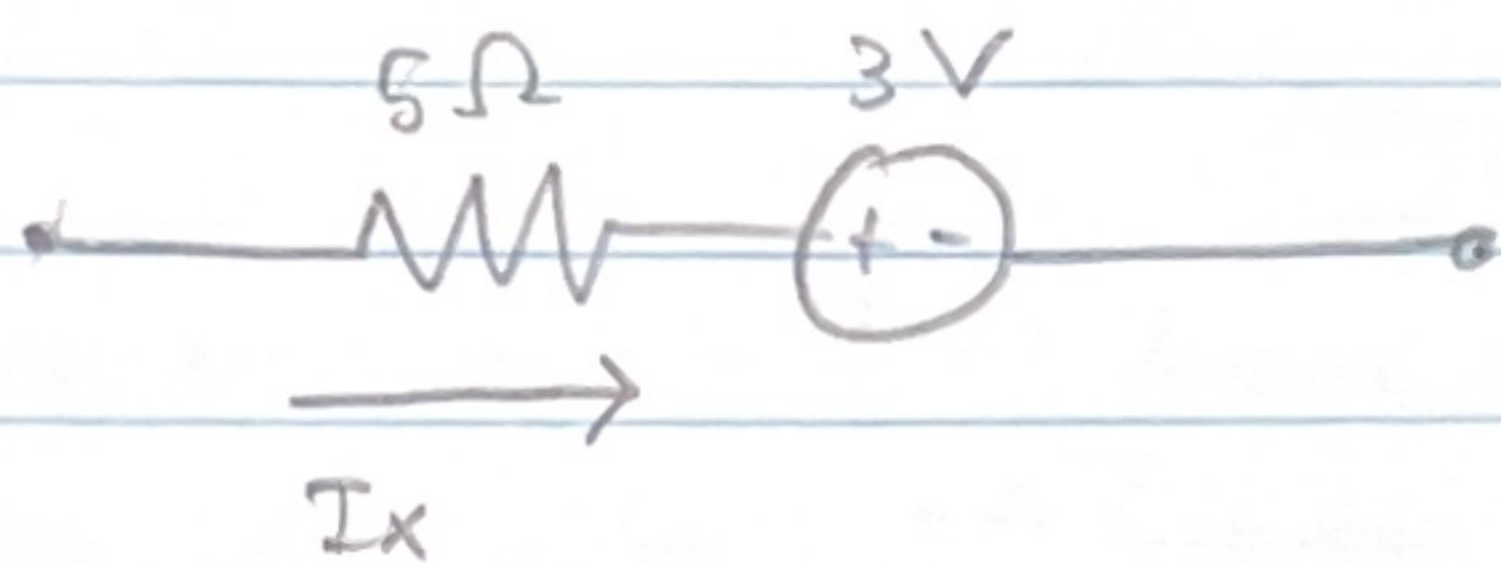

$$I_x = f(V_k, V_m)$$

$$I_x = \frac{V_k - V_m - 3}{5}$$


$$I_x = \frac{V_k}{5} - \frac{V_m}{5} - \frac{3}{5}$$

$$a = \frac{1}{5}$$

$$b = -\frac{1}{5}$$

$$c = -\frac{3}{5}$$

$$p = 0.024$$

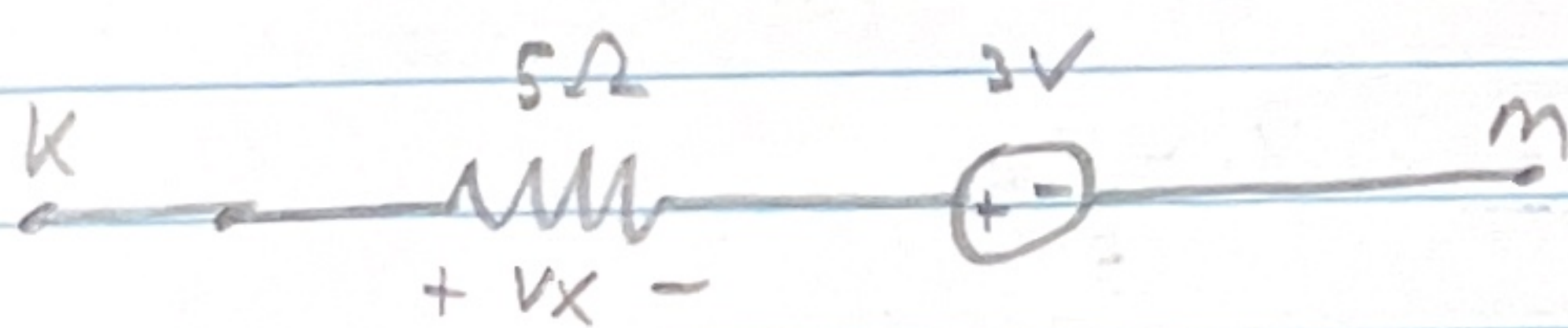

$$V_m + 3 + V_x = V_k$$

$$a = -1$$

$$b = 1$$

$$V_m + 3 + V_x - V_k = 0$$


$$c = 3$$

Modified Nodal Analysis

Unknowns

- ① Voltages of tree nodes (KCL)
- ② Controlling Variables (CTL)
- ③ Evil currents (EVL)

9/28/19
LEC

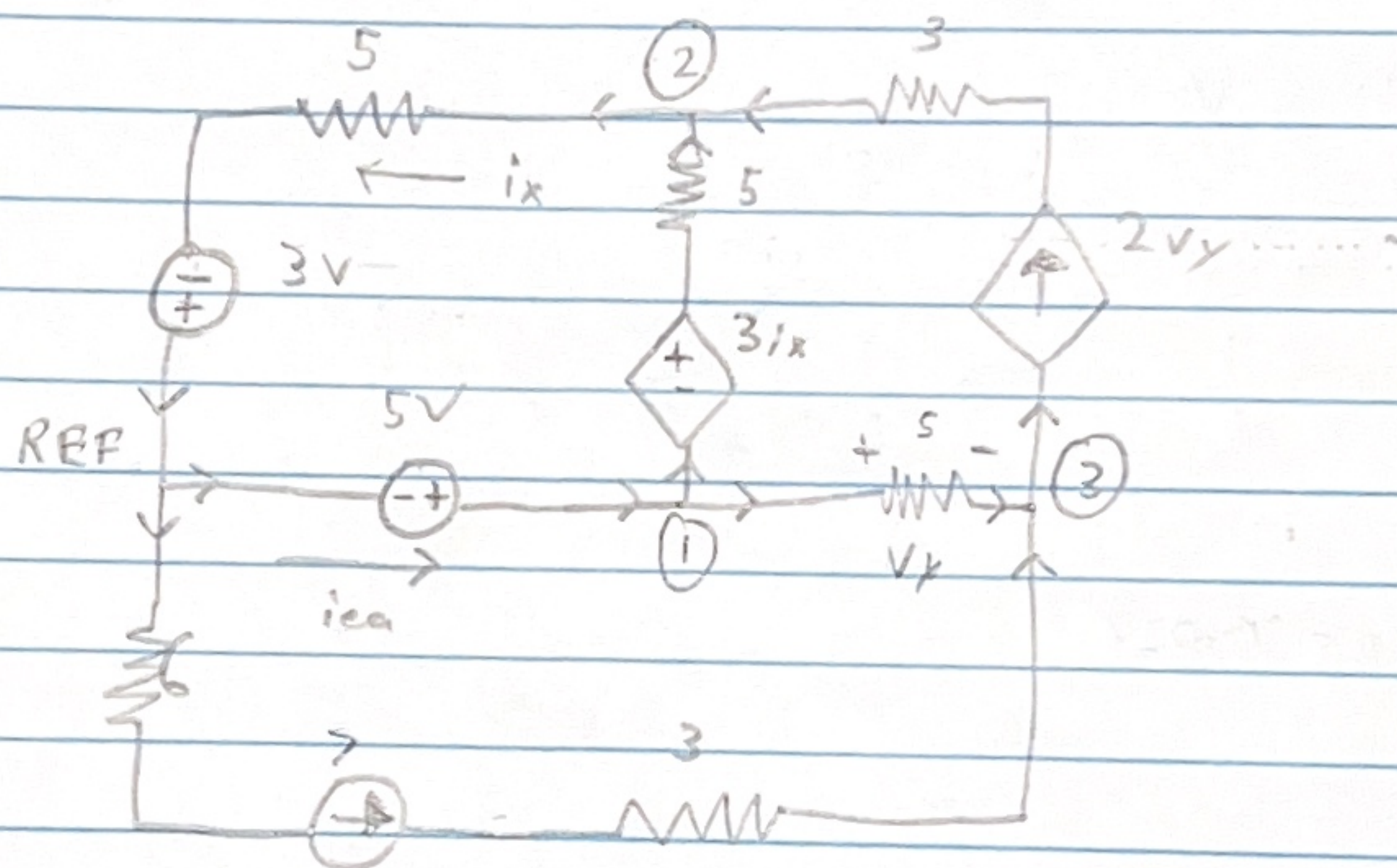

$$N_1: i_{ea} = \frac{V_1 - V_2}{5} + \frac{V_1 - V_2}{5}$$

$$V_2: \frac{V_1 - V_2}{5} + 2V_y = i_x$$

$$V_3: \frac{V_1 - V_3}{5} + 7 = 2V_y$$

$$CTL_1: V_1 - V_y = V_3$$

$$CTL_2: i_x = \frac{V_2 - V_{ref} + 3}{5}$$

$$V_1 = 5$$

$$A \quad V_2 = 14$$

$$B \quad V_3 = 2.4$$

$$C \quad i_x = 3.4$$

$$D \quad V_y = 2.6$$

$$F \quad i_{ea} = \frac{-3.6}{5} = -0.72 \text{ A}$$

$$0.335 \text{ A}$$

$$\frac{V}{IR} \quad I = \frac{V}{R}$$


Thenevin and Norton Equivilants

Thenevin equivilant $\rightarrow V_{source}$


Norton equivilant $\rightarrow I_{source}$

4 new Ideal Elements


① open circuit eqn: $i = 0$

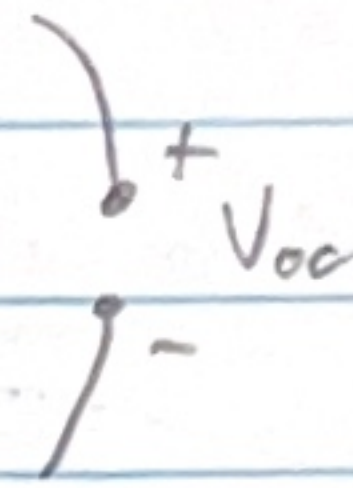


② Short circuit eqn: $V = 0$

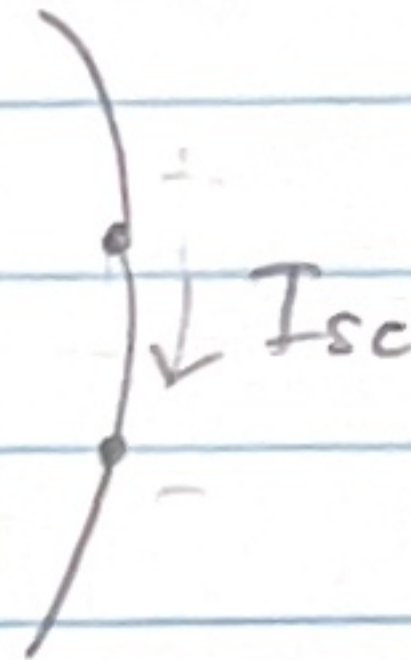

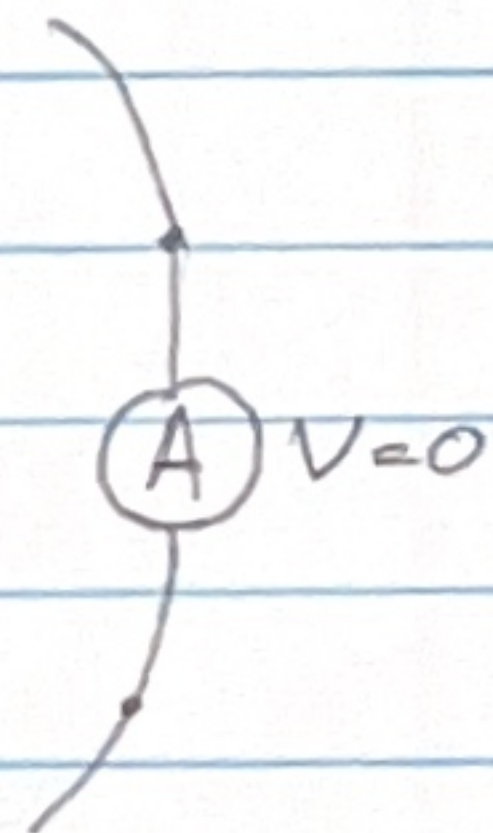③ Ideal Ammeter $\rightarrow$ shows current through it
(special short circuit)




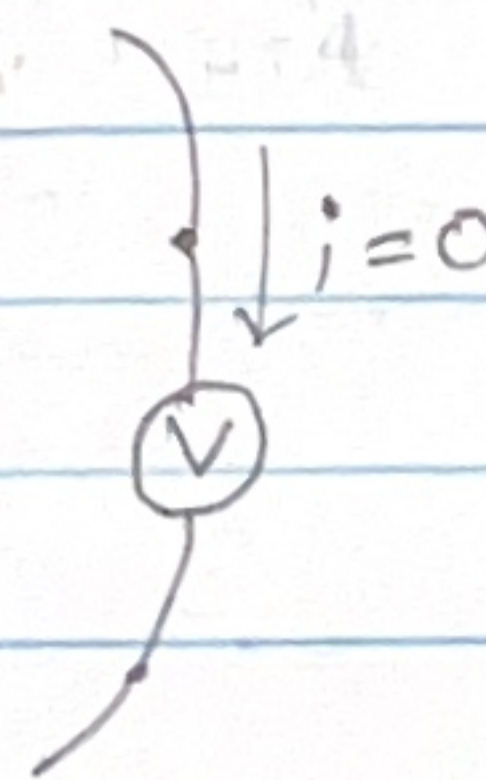④ Ideal Voltmeter $\rightarrow$ shows voltage
(special open circuit)




Classic method

OPEN TEST

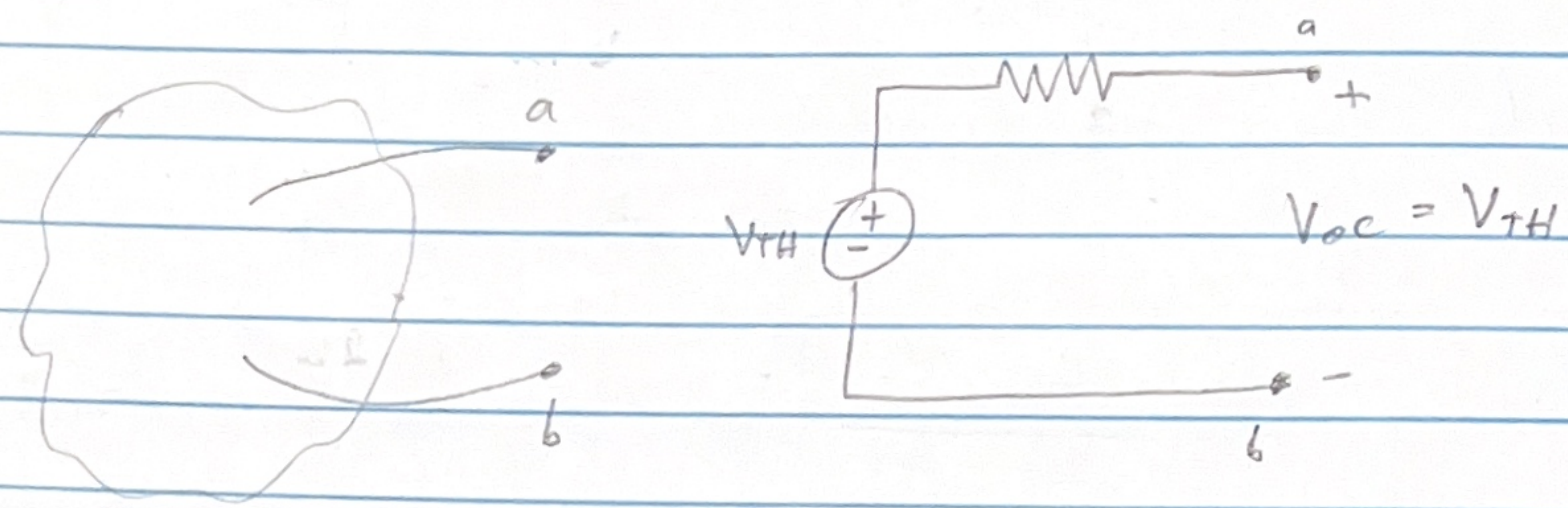


SHORT TEST

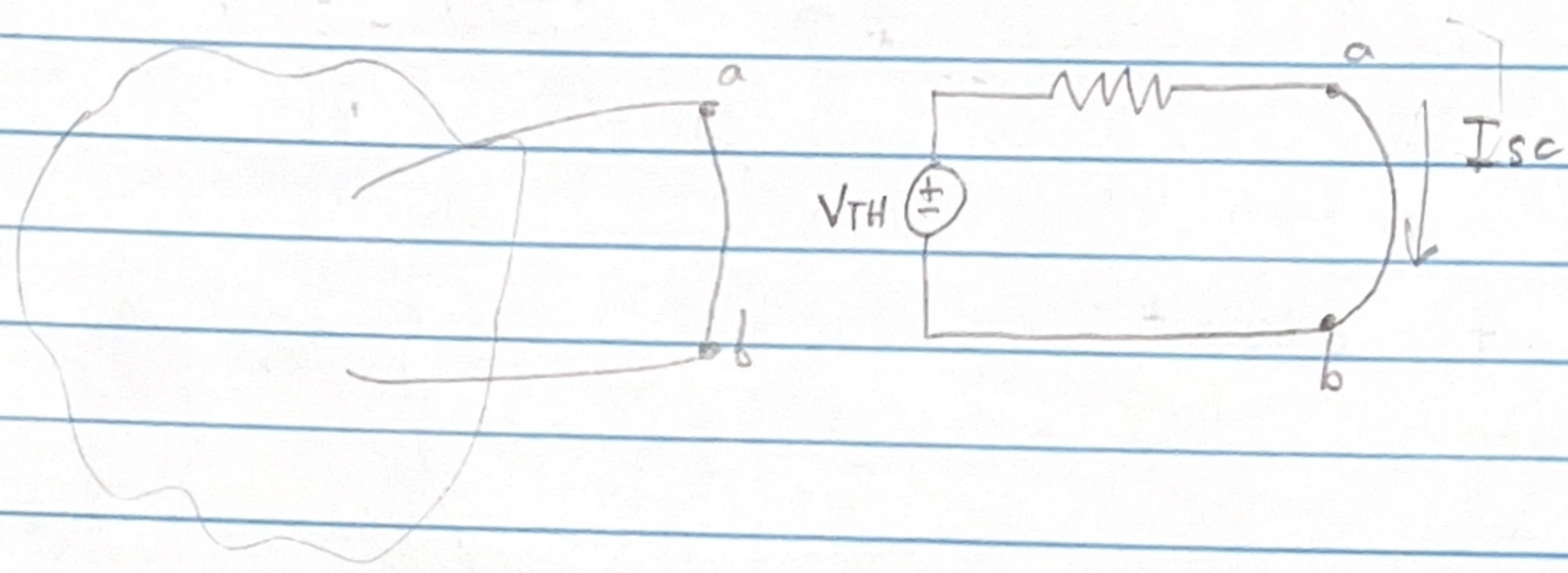

$$I_{SC} = \frac{V_{TH}}{R_{TH}}$$

$$V_{TH} = V_{OC}$$

$$R_{TH} = \frac{V_{TH}}{I_{SC}}$$

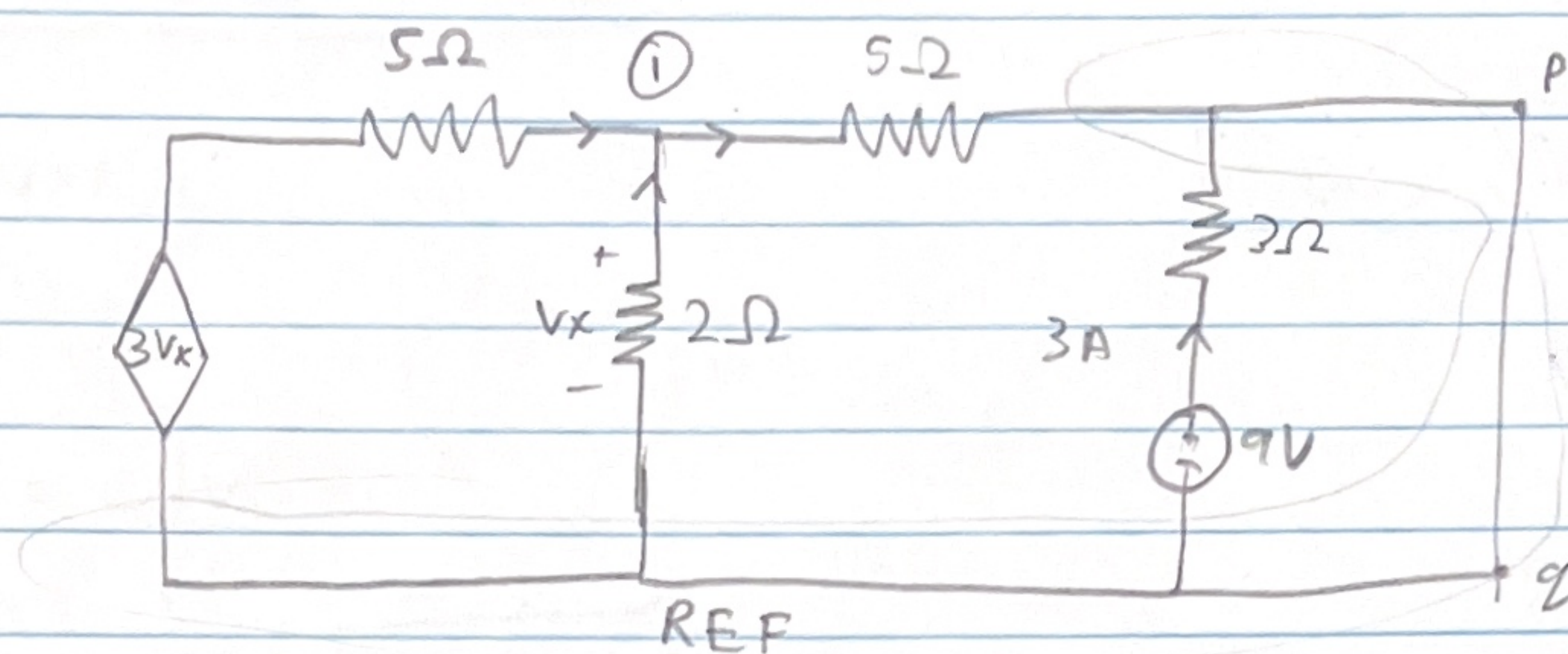

$$V_1: \frac{0 - V_1 + 3V_x}{5} + \frac{0 - V_1}{2} = \frac{V_1 - 0 - 9}{8}$$

$$\text{CTL: } 0 + V_x = V_1$$

$$V_x = 5$$

$$V_1 = 5$$

$$I * R$$

$$\left(\frac{V_1 - V_0 - 9}{8} \right) (5) = -5/2$$

$$\frac{V}{IR}$$

$$I = \frac{V}{R}$$

$$\frac{0 - 5 + 5 + 9}{3} = 3A$$

$$\frac{V_1 - 0}{5} = 1A$$

Maximum power transfer Criterion

10/04/18

LEC

Power formulas


$$P = IV$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

For max power $R_x = R_{TH}$

Transistor

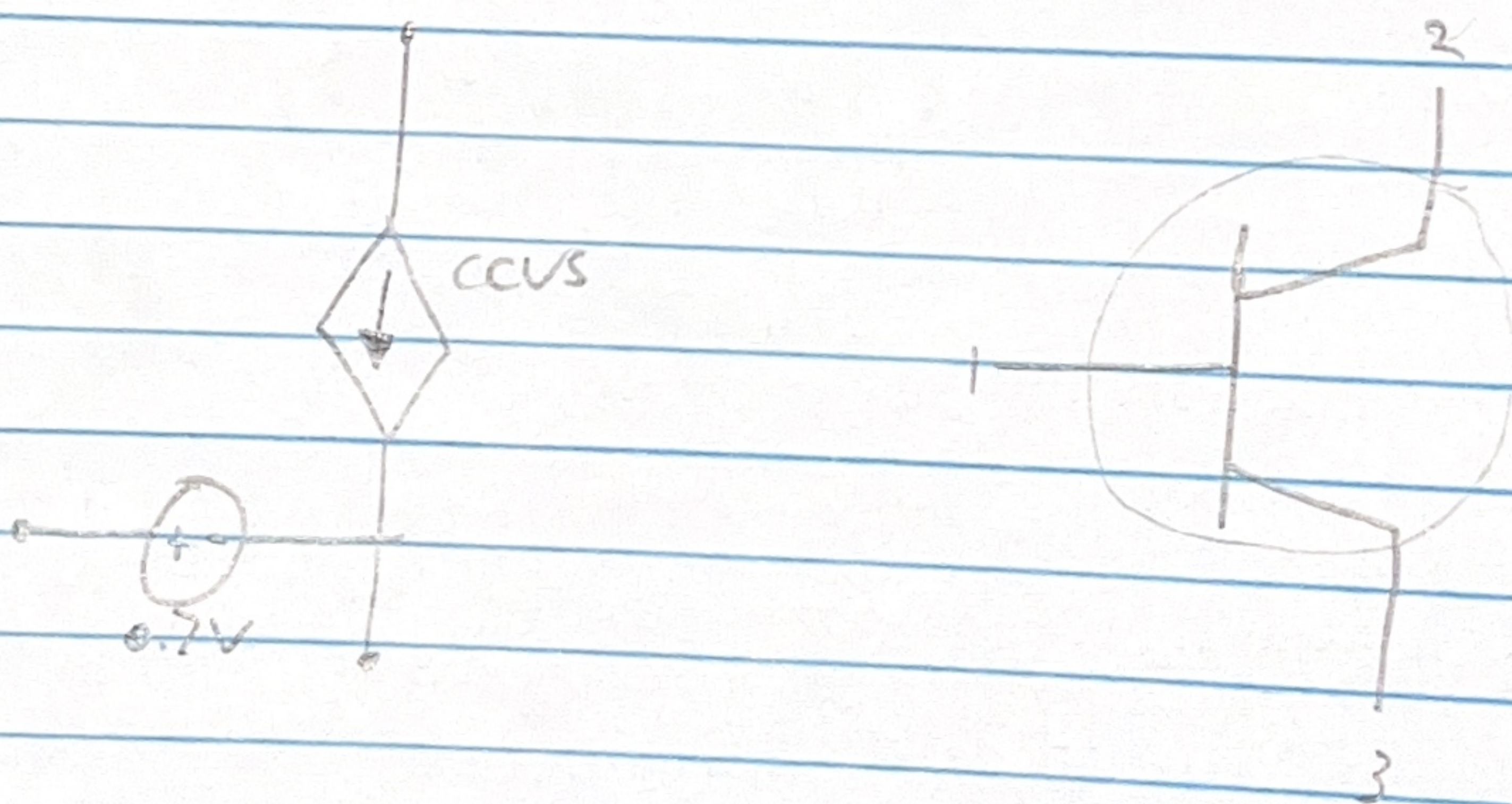


DE order = # of reactive elements

First order Circuits

$$V = L \frac{di}{dt}$$

$$i = C \frac{dv}{dt}$$

RC Circuit

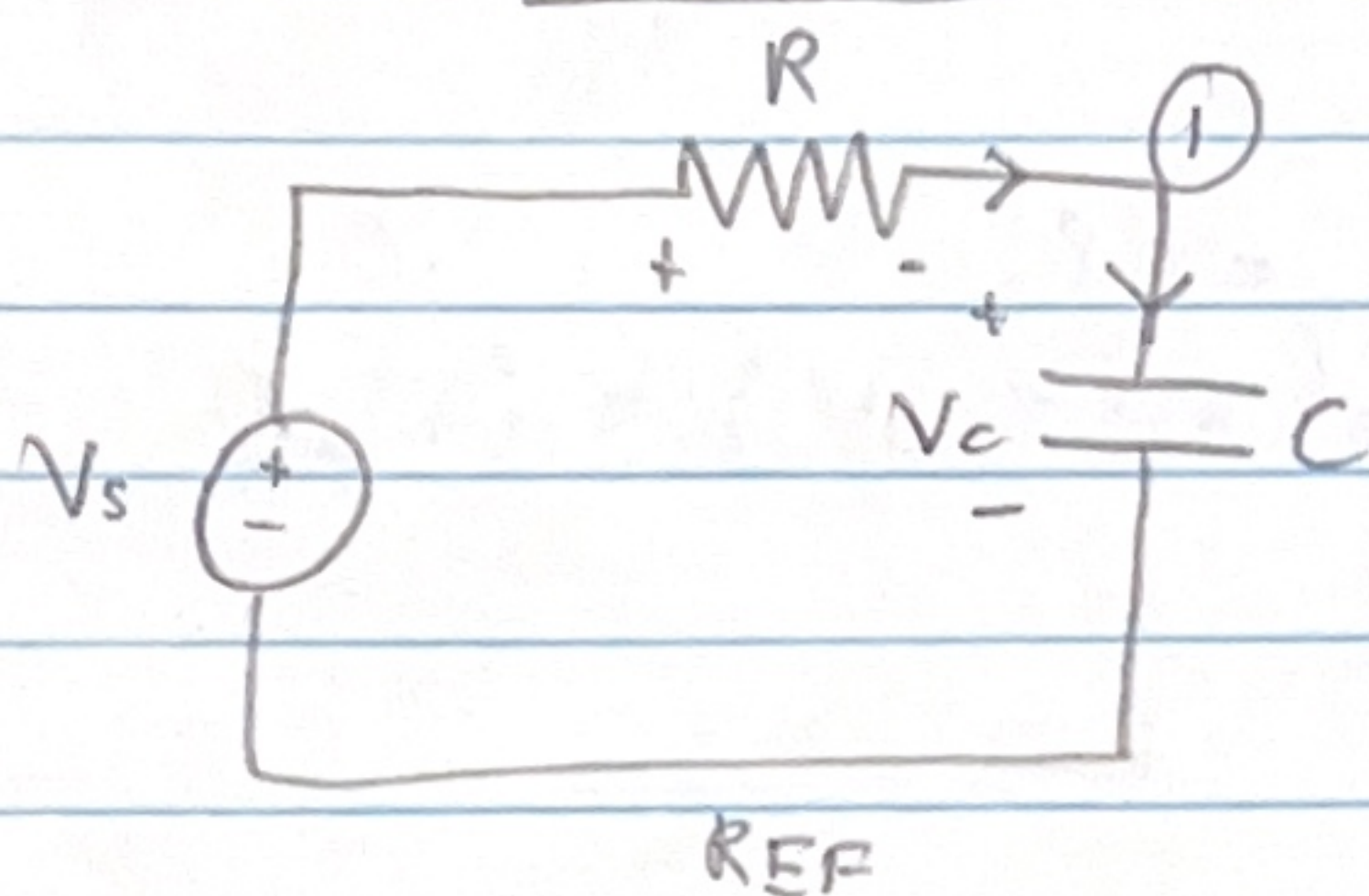

$$V_c = V_i \quad i_c = C \frac{dV_i}{dt}$$

$$\text{KVL: } V_s - Ri - V_c = 0$$

$$\text{KCL: } 0 + V_s - V_i = C \frac{dV_i}{dt}$$

$$V_s - V_i = RC \frac{dV_i}{dt}$$

$$V_s = V_i + RC \frac{dV_i}{dt}$$

constant coefficient 1st order DE

Exponential functions

$$i(t) = Ae^{-t/\tau}$$

$$i(t) = (I_0 - I_f)e^{-t/\tau} + I_f$$

